

Name:
Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, April/May 2018

Course: VHDL
Semester: VIII
Time: 03 hrs.


Code: ELEG-434
Program: B. Tech/EE
Max. Marks: 100

SECTION A

S. No.		Marks	CO
Q 1	Write concurrent code for 8 to 1 Mux using WHEN-ELSE statement	5	CO3
Q2	Explain the Behavioral domain, Structural domain and Physical domain of system to silicon level VLSI Design.	5	CO2
Q3	List out the salient features MAX 7000 series CPLD with neat sketch. And also explain about the structure of CLB's and Slices in the FPGA architecture.	5	CO1
Q4	Derive the circuit for the piece of Verilog code given below and write the code at dataflow level. <pre>module electronics(x,clock,Q1,Q2) input x, clock; output reg Q1, Q2; always@(posedge clock) begin Q1=x; Q2= Q1; end end module</pre>	5	CO4

SECTION B


Q5	Mention all the types of pre-defined data types, operators and data & signal attributes in VHDL. And also Mention the output for the following. i. W <= (0 =>'1', OTHERS => '0'); ii. d'Reverse_range of Signal d:std_logic_vector(7 downto 0); iii. If x<="1001010" then Y<= x sra 4	10	CO1
Q6	Write the VHDL code for the following RTL diagram of the SISO shift register. Consider the data"1010" given to SISO shift register, with neat sketch the output graph after simulation and also explain the step by step procedure of data transfer w.r.t clock pulse.	10	CO3

 

Q7	Write 4 bit Parallel adder structural VHDL code using fulladder as component	10	CO3
Q8	<p>Analyze the following design terms in the VLSI design cycle</p> <ul style="list-style-type: none"> a) Architectural Design b) Functional Design c) Logic Design d) Circuit Design e) Physical Design 	10	CO1

SECTION-C

Q9	<p>a) Design the synchronous sequential circuit for the following state graph. Choose flip-flop of your choice</p> <p>b) Write the VHDL code for the design using dataflow model</p> <p>c) Write the Verilog code for the design using structural model</p>	20	CO4
Q10	<p>Analyze the following multiplexer VHDL code carefully and write the simulation test bench for the same with neat graph. And make the necessary changes to the code to make it synthesizable on FPGA.</p> <pre> architecture Behavioral of mux is begin process(a, sel) is begin if(sel(0)<='0' and sel(1)<='0') then y<=a(0); elsif(sel(0)<='1' and sel(1)<='0') then y<=a(1); elsif(sel(0)<='0' and sel(1)<='1') then y<=a(2); elsif(sel(0)<='1' and sel(1)<='1') then y<=a(3); end if; end process; </pre>	20	CO2

 

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, April/May 2018


Course: VHDL
Semester: VIII
Time: 03 hrs.

Code: ELEG-434
Program: B. Tech/EE
Max. Marks: 100

SECTION A

S. No.		Marks	CO
Q 1	List out atleast ten different keywords in VHDL and Verilog HDL's. And also differentiate between ASIC and FPGA design.	5	CO3
Q2	Explain the Gajski's Y-chart system to silicon level VLSI Design with neat sketch.	5	CO1
Q3	Construct the basic layout of SPLD architecture with neat sketch.	5	CO2
Q4	Write the Verilog code and the stimulus for the following Boolean function $x = A + BC + B'D$ $y = B'C + BC'D'$	5	CO4


SECTION B

 Q5	Mention all the types of pre-defined data types, operators and data & signal attributes in VHDL. And also Mention the output for the following. i. $W \leq (0 \Rightarrow '1', OTHERS \Rightarrow '0');$ ii. d'Reverse_range of Signal d:std_logic_vector(7 downto 0); iii. If $x \leq "1001010"$ then $Y \leq x \text{ sra } 4$	10	CO1								
Q6	Observe the following graph carefully, derive the specifications of the system, create the logic, generate the complete VHDL code and the test bench required to get the following system output along with the RTL diagram.  <table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>Name</th> <th>Value</th> </tr> </thead> <tbody> <tr> <td>e</td> <td>1</td> </tr> <tr> <td>clk</td> <td>1</td> </tr> <tr> <td>y[3:0]</td> <td>-2</td> </tr> </tbody> </table>	Name	Value	e	1	clk	1	y[3:0]	-2	10	CO3
Name	Value										
e	1										
clk	1										
y[3:0]	-2										
Q7	Develop 4-bit, 2's complement adder/subtractor using Full adder as component. The control line $M='1'$ performs subtraction and $M='0'$ performs addition.	10	CO3								
Q8	Analyze the following design terms in the VLSI design cycle a) Architectural Design b) Functional Design c) Logic Design d) Circuit Design e) Physical Design	10	CO1								

SECTION C

Q8	a) Design the synchronous sequential circuit for the following state graph. Choose flip-flop of your choice b) Write the VHDL code for the design using dataflow model	20	CO4
----	---	----	-----

 c) Write the Verilog code for the design using structural model



Q10

Analyze the following Decoder VHDL code carefully, insert ICON, ILA and VIO IP cores into the code to implement the same on FPGA hardware.

```

entity decoder is
port(
  a : in STD_LOGIC_VECTOR(1 downto 0);
  b : out STD_LOGIC_VECTOR(3 downto 0));
end decoder;
architecture bhv of decoder is
begin
process(a)
begin
case a is
when "00" => b <= "0001"; when "01" => b <= "0010"; when "10" => b <= "0100";
when "11" => b <= "1000";
end case;
end process;
end bhv;
  
```

20

CO2
