

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, April/May 2018**

**Course: Analog Electronics**  
**Program: B.TECH EE IOT**  
**Time: 03 hrs.**

**Semester: IV**  
**Max. Marks: 100**


**Instructions: All questions are compulsory**

**SECTION A**


S. No.		Marks	CO
Q1.	Analyze the Characteristics of NMOSFET and N type BJT and mention all the operating regions?	5	CO1
Q2.	Draw the transfer and output characteristics of N- channel JFET and elaborate on the input impedance of the JFET.	5	CO1
Q3.	Evaluate the output and input impedance of Voltage shunt and current shunt feedback amplifiers and also draw the block diagram?	5	CO3
Q4.	Determine the output voltage $V_o(t)$ of the given circuit? <div style="text-align: center;"> </div>	5	CO4

**SECTION B**

Q 5	<p>The fixed-bias configuration of Example 6.1 had an operating point defined by <math>V_{GSQ} = 2</math> V and <math>I_{DQ} = 5.625</math> mA, with <math>I_{DSS} = 10</math> mA and <math>V_{GSOFF} = -8</math> V. The network is redrawn as in given figure with an applied signal <math>V_i</math>. The value of <math>y_o</math> is provided as 40<math>\mu</math>S.</p> <p>(a) Determine <math>g_m</math>.            (b) Find <math>r_d</math>.            (c) Determine <math>Z_i</math>.            (d) Calculate <math>Z_o</math>.            (e) Determine the voltage gain <math>A_v</math>.</p>	<b>10</b>	<b>CO2</b>
-----	--	-----------	------------

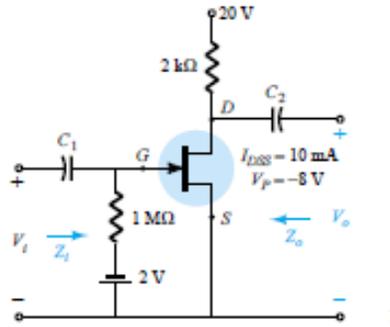


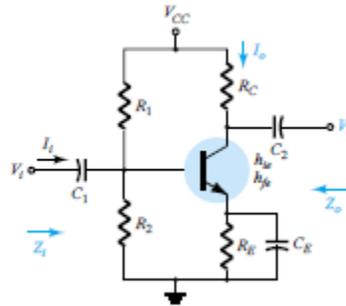Q6. Derive the small signal parameters of the given BJT configuration?




10 CO2

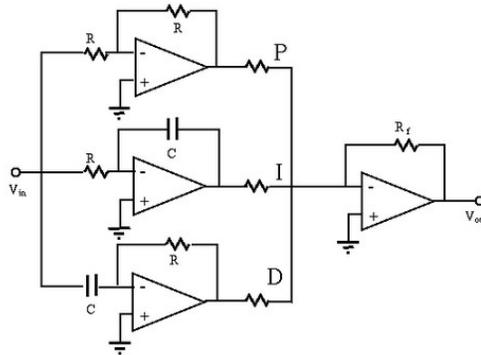Q7. (a) Evaluate the final output of the multistage Opamp configuration?



(b). Input signal is Triangular waveform (only positive amplitude) at non inverting terminal and calculate the final output response of the given Opamp?

10 CO3

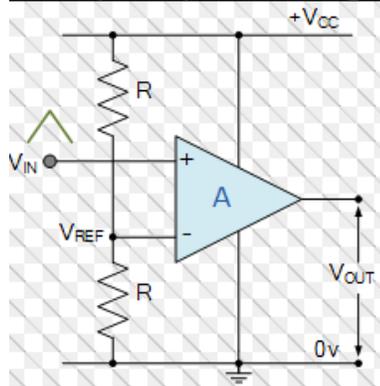


Q8. Consider the given circuit below of MOSFET configuration and find the Value of

10 CO4

resistance  $R_2$ ?

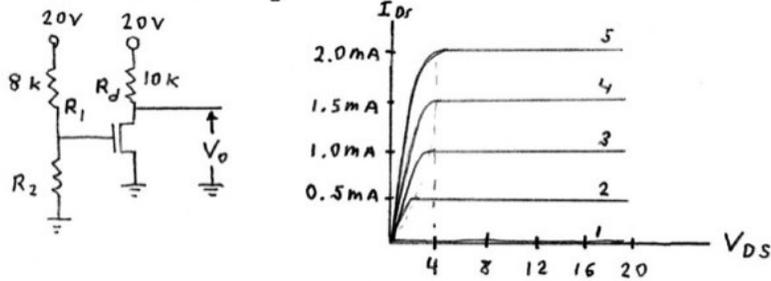IV) Shown below is a MOSFET amplifier and the characteristic curves for the MOSFET. Find  $R_2$  so that  $V_o = 10$  volts.



SECTION-C

Q9. Design a band pass filter Using Operational Amplifiers for the Bandwidth 10 MHz and consider the following ?  
 (a). Highest Frequency of the Bandwidth will be 50Mhz.  
 (b). Draw the final frequency spectrum of the filter.

20

CO2,C  
O3

Q10. (a).Design a self-bias network using a JFET transistor with  $I_{DSS} = 8$  mA and  $V_{gsoff} = -6$  V to have a Q-point at  $I_{DQ} = 4$  mA using a supply of 14 V.  
 (b). Design an circuit such that if the input is  $I(t) = 20u(t)$ , the output will be  $O(t) = -80tu(t)$ .

20

CO3,C  
O4

Name: