

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, May 2019

Programme Name: BT-E&CE Course Name : Analog Electronics II Course Code : ECEG 2014 Nos. of page(s) : 02	Semester : IV Time : 02 hrs Max. Marks: 100
---	--

- Instructions:**
- Attempt all questions.
 - Assume any data if required and indicate the same clearly. Otherwise indicated symbols and notations have their usual meanings.
 - Strike off all unused blank pages.

SECTION A

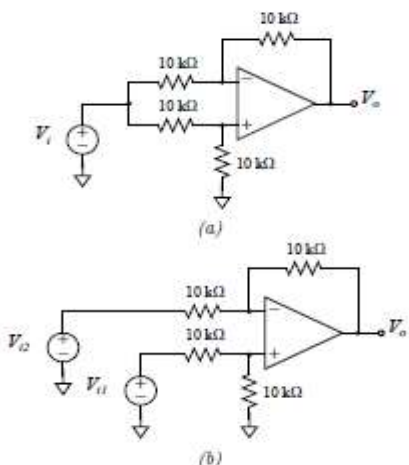
S. No.	Question	Marks	CO
Q1.	Write short notes on virtual ground concept.	5	CO1
Q2.	Discuss why astable multivibrator is also known as free running oscillator.	5	CO2
Q3.	Determine V_{out} for the two connections shown in below Figure 1 . Assume $V_1 = 3V$, $V_a = 2V$ and $V_b = 3V$. <div style="text-align: center; margin: 10px 0;">  </div>	5	CO3

Figure 1

Q4.	With neat block diagram, explain the operation of 8-bit successive approximation register type ADC. What is the maximum conversion time for this type of ADC.	5	CO2
-----	---	---	-----

SECTION B

Q5.	<p>A regenerative comparator (Schmitt Trigger) circuit is shown in Figure 3</p> <p>Derive expressions for upper threshold and lower threshold voltages, V_{UT} and V_{LT} respectively and hence the value of hysteresis voltage V_H. Calculate V_{UT}, V_{LT}, V_H for the given values of $R_1 = 27\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.</p>	10	CO3
-----	--	----	-----

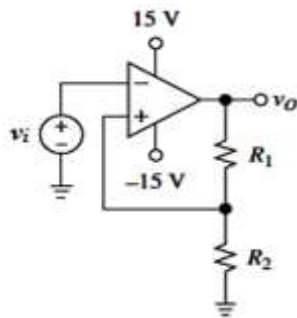


Figure 3

Q6.	<p>A sine wave with 2 V peak-to-peak amplitude and 1 kHz frequency is applied at the input of the circuit. Plot the input and output waveforms. $V_{cc} = +15\text{ V}$</p>	10	CO3
-----	--	----	-----

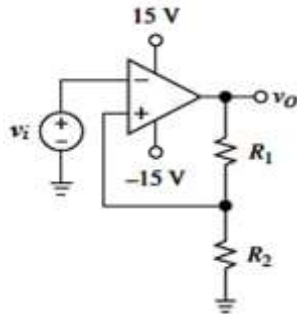


Figure 4

Q7.	Show that the Low pass RC network performs filtering and op-amp provides amplification?	10	CO3
Q8.	Design a circuit using op-amp to produce a square wave output whose output does not have any stable state and the Output has two Quasi-Stable states where output keeps on changing its own from 1state to another state and Vice Versa.	10	CO4

SECTION-C

Q 9	Design an astable multivibrator for an output frequency of 1 kHz but a variable duty cycle of 30% to 70%. Assume $V_{cc}=12\text{V}$.	20	CO4
Q 10	Design a timer, which should turn ON heater immediately after pressing a push button and should hold heater in 'ON-state' for 5 seconds.	20	CO4

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, May 2019

Programme Name: BT-E&CE

Semester : IV

Course Name : Analog Electronics II

Time : 02 hrs

Course Code : ECEG 2014

Max. Marks: 100

Nos. of page(s) : 02

Instructions:

- Attempt all questions.
- Assume any data if required and indicate the same clearly. Otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages.

SECTION A

S. No.		Marks	CO
Q1.	<p>Figure 1 shows the output voltage of an op-amp in response to the step input. Find the slew rate.</p> <p>Figure 1</p>	5	CO2
Q2.	<p>With neat block diagram, explain the operation of 8-bit successive approximation register type ADC.</p>	5	CO1
Q3.	<p>Discuss why astable multivibrator is also known as free running oscillator.</p>	5	CO2
Q4.	<p>Determine V_{out} for the two connections shown in below Figure 2. Assume $V_1 = 3V$, $V_a = 2V$ and $V_b = 3V$.</p>	5	CO3

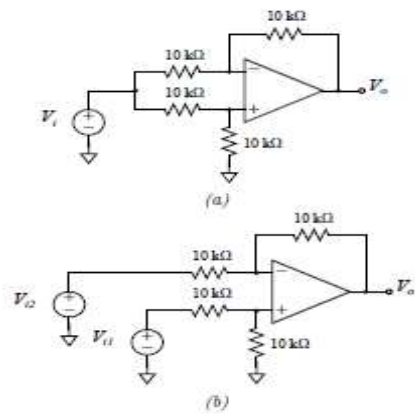


Figure 2

SECTION B

- Q5. Design a circuit using op-amp to produce a square wave output whose output does not have any stable state and the Output has two Quasi-Stable states where output keeps on changing its own from 1state to another state and Vice Versa.
- Q6. Show that the Low pass RC network performs filtering and op-amp provides amplification?
- Q7. A sine wave with 2 V peak-to-peak amplitude and 1 kHz frequency is applied at the input of the circuit. Plot the input and output waveforms. $V_{cc} = +15\text{ V}$

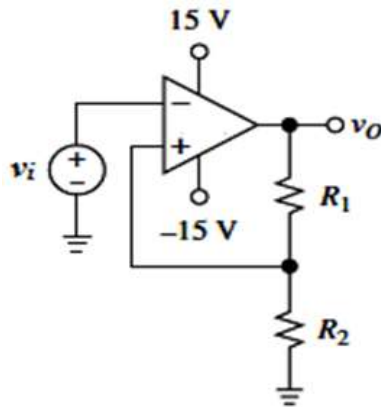


Figure 3

10

CO4


10

CO3

10

CO3

Q8.	<p>A regenerative comparator (Schmitt Trigger) circuit is shown in Figure 4</p> <p>Derive expressions for upper threshold and lower threshold voltages, V_{UT} and V_{LT} respectively and hence the value of hysteresis voltage V_H. Calculate V_{UT}, V_{LT}, V_H for the given values of $R_1 = 27 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$.</p>	10	CO3
SECTION-C			

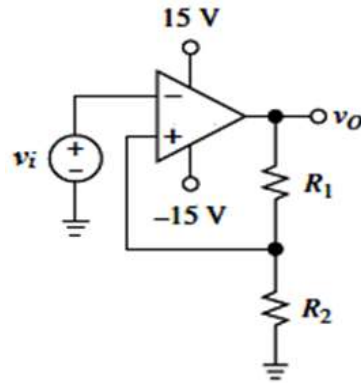

Q 9	Design an astable multivibrator which will flash the electric bulb such that its ON time will be 3 seconds and off time will be 1 seconds.	20	CO4
Q 10	Design a timer, which should turn ON heater immediately after pressing a push button and should hold heater in 'ON-state' for 5 seconds.	20	CO4