


Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2019

Programme Name:	B.Tech (APEG, CERP, ME, APEUP)	Semester :	I
Course Name :	Basic Electronics Engineering	Time :	3Hr
Course Code :	ECEG1002	Max. Marks :	100
Nos. of page(s) :	03		
Instructions :	Attempt all questions from Section (A) and (B) and only one from Section (C).		


SECTION A

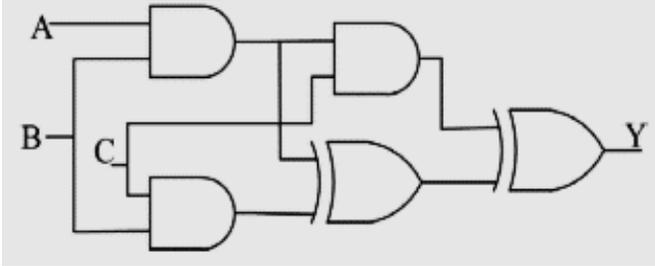S. No.	Question	Marks	CO
Q1	Explain the behavior of diode in forward biasing. Sketch the required circuit diagram and its output V-I characteristic with related terminology.	7	CO1
Q2	Develop the simplified Boolean expression for the following digital circuit: <div style="text-align: center;">  </div>	7	CO4
Q3	What names are applied to the two types of BJT transistors? Sketch the basic construction of each and label the various minority and majority carriers in each.	8	CO3
Q4	Simplify the following Boolean expressions: a) $Y = (A + B + C).(A + B)$ b) $Y = AB + ABC + ABC\bar{C}$	8	CO4

SECTION B

Q5	Explain the concept of dc and ac load line in case of transistor. What is the necessity of operating point and how it is located?	15	CO3
----	---	----	-----

Q6	<p>Consider the transistor ($\beta = 50$) circuit of Figure given below which has a resistance included between emitter and ground. Show that the transistor is operating in active mode. Calculate I_C, I_E and I_B.</p>	15	
----	---	----	--

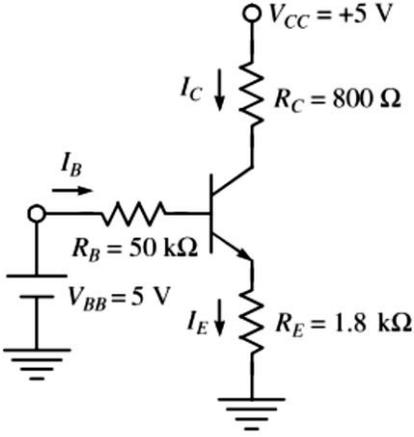


Q7	<p>Convert the following numbers into corresponding number system</p> <ol style="list-style-type: none"> $(A28.1F)_{16} = ()_{10}$ $(378.10)_{10} = ()_8$ $(431.6110)_8 = ()_{16}$ $(1011000111)_2 = ()_{\text{GRAY CODE}}$ $(B65.6A)_{16} = ()_8$ $(101011.1001)_2 = ()_{16}$ 	15	CO4
----	--	----	-----

SECTION C

Note: Attempt any one of the following:

Q8	<p>Given the information provided in Fig. determine:</p> <ol style="list-style-type: none"> β V_{CC}. R_B. 	25	CO3
----	--	----	-----

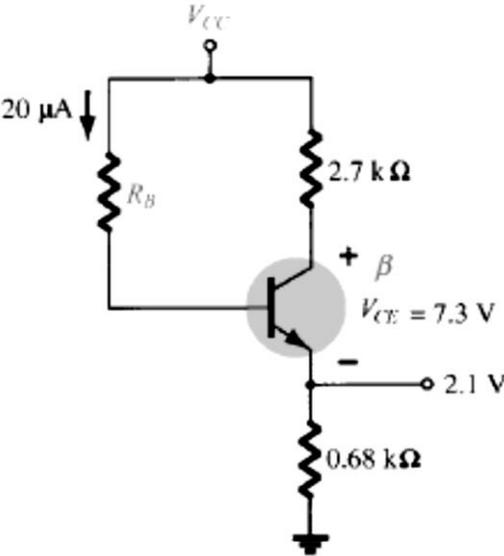

Q9

Use the Karnaugh map method to implement the minimum SOP expression for the logic function specified in truth Table. Also solve the problem for a situation in which the last six binary combinations are not allowed.

Inputs				Output
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

CO4