

Name:	 UPES UNIVERSITY WITH A PURPOSE
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2019

Course: Electric Motors & Drives
Program: M Tech Rotating Equipment
Course Code: EPEC 7008
Instructions: Answer all Questions

Semester: I sem
Time 03 hrs.
Max. Marks: 100

SECTION A

S. No.	Answer all Questions	Marks	CO
Q 1	Describe the advantages and disadvantages of AC drives	5	CO1
Q 2	A separately excited dc motor, operating from a single phase half-controlled bridge at a speed of 1600 rpm, has an input voltage of $340 \sin 314t$ and a back emf 120V. The SCRs are fired symmetrically at $\alpha=45^\circ$ in every half cycle and the armature has a resistance of 2 ohms. Calculate the average armature current and the motor torque.	5	CO2
Q 3	Explain the purpose of free-wheeling diode and how it effects the dc circuit with RL load.	5	CO2
Q 4	Define latching and holding currents as applicable to an SCR. Show these currents on its static I-V characteristics.	5	CO1

SECTION B

Q 5	A dc chopper is used for regenerative braking of a separately excited dc motor. The dc supply voltage is 400 V. the motor $r_a= 0.2$ ohms, $K_m= 1.2$ V-s/rad. The average armature current during regenerative braking is kept constant at 300 A with negligible ripple. For a duty cycle of 60% for a chopper, determine (a) power returned to the dc supply (b) minimum and maximum permissible braking speeds.	10	CO3
Q 6	Describe regenerative braking of a chopper fed separately excited DC motor. Illustrate with circuit diagram and relevant wave forms.	10	CO2
Q 7	A 415 V, 50 Hz, 4-pole, star connected synchronous motor has $X_s= 1.5$ ohms. Load torque, proportional to speed is 300 Nm at synchronous speed. The speed of the motor is lowered by keeping V/f constant and maintaining 0.8 pf leading by field control. For the motor operation at 840 rpm, calculate (a) supply voltage (b) armature current (c) excitation voltage (d) load angle and ϵ pull-out torque. Neglect rotational losses.	10	CO3
Q 8	Describe the stator frequency control for the speed control of a three-phase induction motor. Derive the expressions for motor torque and the slip at which it occurs. State the various assumptions made.	10	CO2
(OR)			
Q 8	Discuss the effect of saturation on the speed -torque characteristics of three phase induction motor obtained by stator frequency control method.	10	CO2

SECTION-C

Q 9	<p>(a) Explain the two methods of speed control normally employed for DC motors. Sketch the characteristics of a separately excited DC motor based on these two methods and indicate constant- Torque drive and constant power drive.</p> <p>(b) A separately excited dc motor is supplied from 230V, 50 Hz source through a single-phase half wave-controlled converter. Its field is fed through single phase semi converter with zero degree firing angle delay. Motor resistance $r_a=0.45$ ohms and motor constant $K_m= 0.55$ V-sec/rad. For rated load torque of 25 Nm at 1200 rpm and for continuous ripple free currents, determine</p> <p>(i) Firing angle delay of the armature converter</p> <p>(ii) RMS value of thyristor and freewheeling diode currents</p> <p>(iii) Input power factor of the armature converter.</p>	20	CO4
	(OR)		
Q 9	<p>(a) Describe the basic performance equations for a DC series motor. Sketch the characteristics of this motor indicating the two regions of constant- Torque mode and constant power mode</p> <p>(b) The speed of a 20 kW, 220 V, 1000 rpm dc series motor is controlled using a single-phase half-controlled bridge converter. The combined armature and field resistance is 0.22 ohms. Assuming continuous and ripple free motor current and speed of 1000 rpm and $k=K_aC= 0.015$ Nm/A², determine (a) motor current (b) motor torque and (c) input power factor for a firing angle $\alpha= 45^\circ$. Ac voltage is 240 V.</p>	20	CO4
Q 10	<p>A dc battery of constant EMF 'E' is charged through a resistor in a single-phase half-controlled diode rectifier circuit for source voltage of 230V, 50 Hz and for $R= 12$ohms, $E=115$ V.</p> <p>(i) Find the value of average charging current</p> <p>(ii) Find the power supplied to battery and the dissipated in the resistor</p> <p>(iii) Calculate supply power factor</p> <p>(iv) Find the charging time in case battery capacity is 1000 Wh.</p>	20	CO4