

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES  
End Semester Examination, December 2019

Course: Analog Electronics (ECEG 2027)

Semester: III


Program: B. Tech ELE



Time: 03 hrs.

Max. Marks: 100

Instructions: Attempt all questions.  
Diagrams must be neat and clean

SECTION A

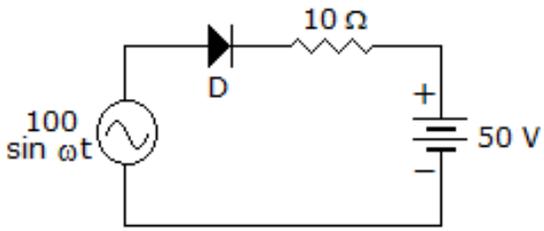S. No.		Marks	CO
Q 1	Discuss the action of an <b>operational amplifier</b> as an <b>integrator</b> .	5	CO3
Q 2	Describe the action of a <b>transistor</b> as an <b>amplifier</b> . What will happen to its action, if the <b>doping</b> concentration of <b>collector is same as emitter</b> ?	5	CO2
Q 3	 <p>In the circuit of figure the diode, find the <b>condition</b> when the <b>diode will operate</b>.</p>	5	CO1
Q 4	What best describe the <b>circuit</b> given below. Draw the <b>output waveform</b> , the input waveform is given below. What will be happen to the output if the <b>polarity</b> of the <b>diode is reversed</b> ?	5	CO1

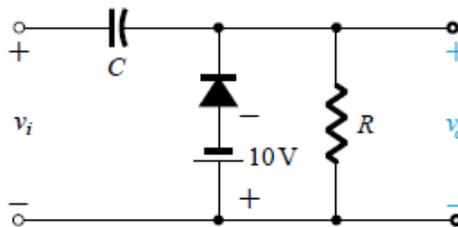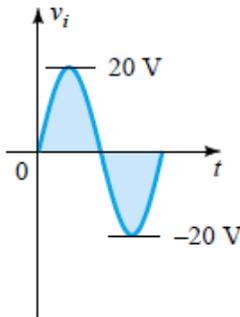


**SECTION B**

Q 5 Describe the working of a **JFET transistor**, with schematic representation of distribution of  $V_{DS}$  of 8 V and  $V_{GG}$  of -1V. What will happen to channel distribution when  $V_{GG}$  becomes +1 V.

**10 CO2**

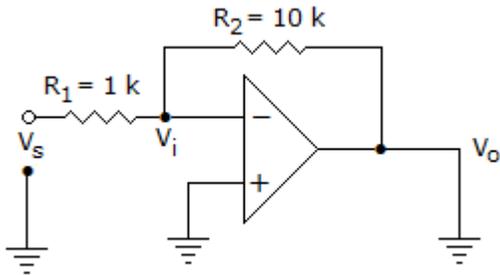
Q 6 Analyze the **op-amp circuit** shown in the figure has an open loop gain to 100. Calculate the **closed loop ratio** ( $V_o/ V_s$ ).




**10 CO4**

Q 7 Determine the **current** through each diode if

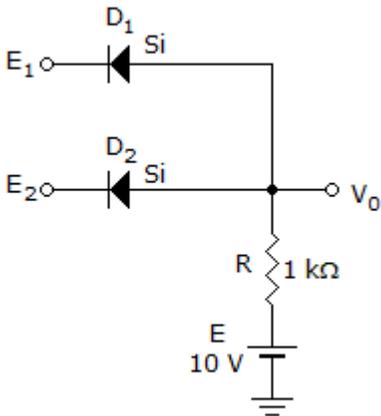- (i)  $E_1 = E_2 = 0$  V,
- (ii)  $E_1 = E_2 = 5$  V.



**10 CO1**

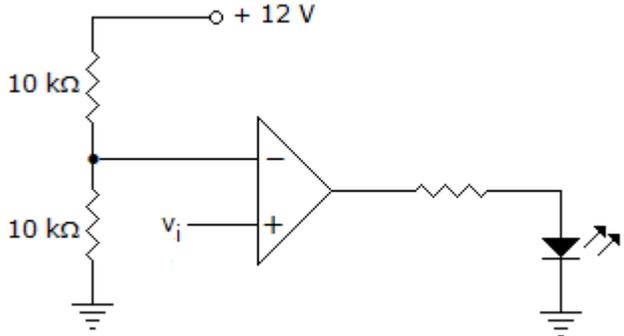Q 8	<p>In the circuit given below, calculate the value of <math>V_i</math> for the LED to be on.</p> 		CO4
-----	--	--	-----

**SECTION-C**

Q 9	<p>Design an <b>AC connection of differential amplifier circuit</b> and determine the single ended output voltage of the circuit with the following specification  <math>V_{CC} = 9\text{ V}</math>, <math>R_C = 69\text{ k}\Omega</math>, <math>R_E = 61\text{ k}\Omega</math>, <math>V_{in} = 2\text{ mV}</math>.</p> <p style="text-align: center;"><b>OR</b></p> <p>Design a <b>three stage amplifier</b>, using operational amplifier, providing outputs that are 10, 20 and 40 times larger than the input. The feedback resistor for all the three circuits are <math>540\text{ k}\Omega</math>.</p>	20	CO4
Q 10	<p>Design a <b>Band Pass Filter</b> circuit using <b>two</b> operational amplifier.</p> <p>Also determine the cut off frequencies of the filter with the following specifications:  <math>R_1 = R_2 = 10\text{ k}\Omega</math>, <math>C_1 = 0.1\text{ }\mu\text{F}</math>, <math>C_2 = 0.002\text{ }\mu\text{F}</math>.</p> <p>Draw the <b>BODE</b> plot for the lower cut off frequency.</p>	20	CO3