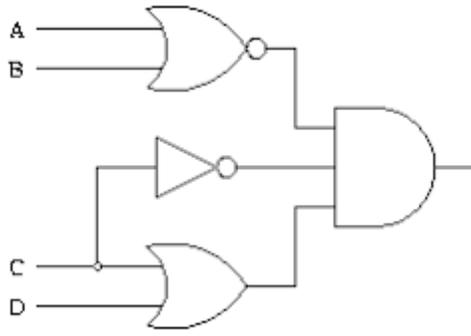


Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2019

Course: Digital Systems and Applications Program: B.Sc. Physics (H) Course Code: PHYS2003	Semester: III Time 03 hrs. Max. Marks: 100
--	---

SECTION A (All Questions are compulsory)

S. No.		Marks	CO
Q 1	Convert the Boolean expression $A\bar{B}C + \bar{B}C\bar{D} + A\bar{C}D$ to a standard sum of products (SOP) form.	4	CO2
Q 2	Using 2's complement representation, add +37 to -115.	4	CO1
Q 3	Determine the Boolean expression for the output of the logic circuit shown in the figure below. <div style="text-align: center; margin: 10px 0;">  </div>	4	CO2
Q 4	Write a short note on ALU.	4	CO4
Q 5	Differentiate between ROM and RAM.	4	CO4

SECTION B

Q 5	Using a K-map, simplify the following function and realize it using NAND gate: $f(A, B, C, D) = \sum(1,4,6,7,8,9,10,11,15)$	10	CO2
Q 6	Draw the schematic of a 4 bit left shift register with parallel loading using D Flip-Flops. Also demonstrate its working.	10	CO3
Q 7	Draw the block diagram of a CRO and explain the function of each block? OR Demonstrate the working of an integrated circuit? Discuss the relative advantages and disadvantages of ICs over discrete assembly.	10	CO1
Q 8	A 555 timer is used as an astable multivibrator. If $R_A=4.7k\Omega$, $R_B=10k\Omega$ and $C=680pF$, determine its frequency and duty factor.	10	CO3

SECTION-C

Q 9	<p>a) Draw a master-slave J-K Flip Flop system. Explain the various operation stages. How is the race around condition eliminated by using this Flip Flop? (10)</p> <p>b) Explain the working of 555 timer as monostable multivibrator with the help of circuit diagram and waveform. (10)</p>	20	CO3
Q 10	<p>a) Draw a labelled pin out diagram of a 8085 microprocessor and explain the function of each pin. (15)</p> <p>b) Describe the various flags used in 8085 microprocessor and show their bit positions (5)</p> <p style="text-align: center;">OR</p> <p>Explain in detail the instruction set of the 8085 microprocessor. (20)</p>	20	CO4