

Name:  
Enrolment No:



**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**Supplementary Examination, January 2020**

**Course: Basic Electronics Engineering**  
**Program: B.Tech CSE - B.Tech CSE – BAO, CCVT, GG, IT, BT**  
**Course Code: PHYS1003**

**Semester: II**  
**Time : 02 hrs.**  
**Max. Marks: 100**

**Instructions:** 1) Assume any missing data

**SECTION A (40 marks)**

S. No.		Marks	CO
Q 1	The most commonly used semiconductor is ..... <ul style="list-style-type: none"> <li>• Germanium</li> <li>• Silicon</li> <li>• Carbon</li> <li>• Sulphur</li> </ul>	1	CO1
Q2	A pentavalent impurity has ..... Valence electrons <ul style="list-style-type: none"> <li>• 3</li> <li>• 5</li> <li>• 4</li> <li>• 6</li> </ul>	1	CO1
Q3	An n-type semiconductor is ..... <ul style="list-style-type: none"> <li>• Positively charged</li> <li>• Negatively charged</li> <li>• Electrically neutral</li> <li>• None of the above</li> </ul>	1	CO1
Q4	"Forward biasing a pn junction diode,..... the width of depletion layer." <ul style="list-style-type: none"> <li>• Decreases</li> <li>• Increases</li> <li>• Remains the same</li> <li>• None of the above</li> </ul>	1	CO1
Q5	A reverse bias pn junction has ..... <ul style="list-style-type: none"> <li>• Very narrow depletion layer</li> <li>• Almost no current</li> <li>• Very low resistance</li> <li>• Large current flow</li> </ul>	1	CO1
Q6	A pn junction acts as a ..... <ul style="list-style-type: none"> <li>• Controlled switch</li> <li>• Bidirectional switch</li> </ul>	1	CO1

	<ul style="list-style-type: none"> <li>• Unidirectional switch</li> <li>• None of the above</li> </ul>		
Q7	<p>The battery connections required to forward bias a pn junction are .....</p> <ul style="list-style-type: none"> <li>• Positive terminal to p and negative terminal to n</li> <li>• Negative terminal to p and positive terminal to n</li> <li>• Negative terminal to p and negative terminal to n</li> <li>• Positive terminal to p and positive terminal to n</li> </ul>	1	CO1
Q8	<p>Which of the following doping generates a P-type semiconductor?</p> <ul style="list-style-type: none"> <li>• Germanium and boron</li> <li>• Germanium and phosphorus</li> <li>• Germanium and antimony</li> <li>• Silicon and Germanium</li> </ul>	1	CO1
Q9	<p>In forward biasing of the p-n junction..</p> <ul style="list-style-type: none"> <li>• the positive terminal of the battery is connected to p-side and the negative terminal of the battery is connected to n-side and depletion region becomes thin.</li> <li>• the positive terminal of the battery is connected to n-side and the negative terminal of the battery is connected to p-side and depletion region becomes thin.</li> <li>• the positive terminal of the battery is connected to n-side and the negative terminal of the battery is connected to p-side and depletion region becomes thick.</li> <li>• the positive terminal of the battery is connected to p-side and the negative terminal of the battery is connected to n-side and depletion region becomes thick.</li> </ul>	1	CO1
Q10	<p>Which of the following circuits would require the least amount of filtering?</p> <ul style="list-style-type: none"> <li>• A half-wave rectifier</li> <li>• A full-wave rectifier</li> <li>• A bridge rectifier</li> <li>• A full-wave rectifier and a bridge rectifier</li> </ul>	1	CO1
Q11	<p>Maximum efficiency of bridge full wave rectifier</p> <ul style="list-style-type: none"> <li>• 81.20%</li> <li>• 40.60%</li> <li>• 25%</li> <li>• 100%</li> </ul>	1	CO1
Q12	<p>The basic purpose of filter is to :</p> <ul style="list-style-type: none"> <li>• minimize variations in ac input signal</li> <li>• suppress harmonics in rectified output</li> <li>• stabilize dc output voltage</li> <li>• remove ripples from the rectified output</li> </ul>	1	CO1
Q13	<p>A half wave rectifier is equivalent to :</p>	1	CO1


	<ul style="list-style-type: none"> <li>• clamper circuit</li> <li>• a clamper circuit with negative bias</li> <li>• Clipper</li> <li>• a clamper circuit with positive bias</li> </ul>		
Q14	<p>"If the doping level in a diode is increased, the width of depletion layer"</p> <ul style="list-style-type: none"> <li>• remains the same</li> <li>• is increased</li> <li>• is decreased</li> <li>• none of the above</li> </ul>	1	CO1
Q15	<p>The number of depletion layers in a transistor is</p> <ul style="list-style-type: none"> <li>• four</li> <li>• three</li> <li>• two</li> <li>• one</li> </ul>	1	CO2
Q16	<p>Which rectifier requires four diodes?</p> <ul style="list-style-type: none"> <li>• Full-wave bridge circuit</li> <li>• Half-wave voltage doublers</li> <li>• Full-wave voltage doublers</li> <li>• None of the above</li> </ul>	1	CO2
Q17	<p>The main job of a voltage regulator is to provide a nearly ..... output voltage.</p> <ul style="list-style-type: none"> <li>• constant</li> <li>• fluctuating</li> <li>• sinusoidal</li> <li>• smooth</li> </ul>	1	CO2
Q18	<p>The base of a transistor is ..... doped</p> <ul style="list-style-type: none"> <li>• Heavily</li> <li>• moderate</li> <li>• lightly</li> <li>• all of the above</li> </ul>	1	CO2
Q19	<p>In a PNP transistor the current carriers are .....</p> <ul style="list-style-type: none"> <li>• acceptor ions</li> <li>• donor ions</li> <li>• free electrons</li> <li>• holes</li> </ul>	1	CO2
Q20	<p>A transistor is a ..... Controlled device</p> <ul style="list-style-type: none"> <li>• current</li> <li>• voltage</li> <li>• both current and voltage</li> <li>• None of the above</li> </ul>	1	CO2
Q21	<p>In a transistor base current is ..... of emitter current</p>	1	CO2

	<ul style="list-style-type: none"> <li>• 5%</li> <li>• 25%</li> <li>• 75%</li> <li>• 99%</li> </ul>		
Q22	<p>The input impedance of a transistor is.....</p> <ul style="list-style-type: none"> <li>• high</li> <li>• low</li> <li>• very high</li> <li>• zero</li> </ul>	1	CO2
Q23	<p>Which of the following holds true for a transistor</p> <ul style="list-style-type: none"> <li>• <math>I_C = I_E + I_B</math></li> <li>• <math>I_B = I_E + I_C</math></li> <li>• <math>I_E = I_C - I_B</math></li> <li>• <math>I_E = I_B + I_C</math></li> </ul>	1	CO2
Q24	<p>The value of <math>\alpha</math> in a transistor is.....</p> <ul style="list-style-type: none"> <li>• more than 1</li> <li>• equal to 1</li> <li>• less than 1</li> <li>• all of the above</li> </ul>	1	CO2
Q25	<p>"In a transistor, <math>I_C = 100</math> mA and <math>I_E = 100.2</math> mA. The value of <math>\beta</math> is ....."</p> <ul style="list-style-type: none"> <li>• 100</li> <li>• 50</li> <li>• 0.2</li> <li>• 200</li> </ul>	1	CO2
Q26	<p>The voltage gain in a transistor connected in ..... arrangement is the highest</p> <ul style="list-style-type: none"> <li>• common base</li> <li>• common collector</li> <li>• common emitter</li> <li>• None of the above</li> </ul>	1	CO2
Q27	<p>The arrow in the symbol of a transistor indicates the directions of.....</p> <ul style="list-style-type: none"> <li>• electron current in the emitter</li> <li>• electron current in the collector</li> <li>• hole current in the emitter</li> <li>• donor ion current</li> </ul>	1	CO2
Q28	<p>A heat sink is generally used with a transistor to .....</p> <ul style="list-style-type: none"> <li>• increase the forward current</li> <li>• decrease the forward current</li> <li>• compensate for excessive doping</li> <li>• prevent excessive temperature ris</li> </ul>	1	CO2
Q29	<p>A Voltage divider bias provides.....</p> <ul style="list-style-type: none"> <li>• unstable operating point</li> </ul>	1	CO2


	<ul style="list-style-type: none"> <li>• stable operating point</li> <li>• a Q point that varies with temperature</li> <li>• all of the above</li> </ul>		
Q30	<p>The phase difference between o/p and i/p for a common collector amplifiers is</p> <ul style="list-style-type: none"> <li>• 270 degrees</li> <li>• 180 degrees</li> <li>• 90 degrees</li> <li>• 0 degrees</li> </ul>	1	CO2
Q31	<p>In which region transistor acts as a switch?</p> <ul style="list-style-type: none"> <li>• Active region</li> <li>• Cut-off region</li> <li>• saturated region</li> <li>• saturated &amp; active region</li> </ul>	1	CO2
Q32	<p>Which of the following is valid for both P-N-P as well as N-P-N transistor</p> <ul style="list-style-type: none"> <li>• The emitter injects holes into the base region</li> <li>• The electrons are the minority carriers in the base region</li> <li>• The EB junction is forward biased for active operation</li> <li>• "When a biased in the active region, current flows into their emitter terminal"</li> </ul>	1	CO2
Q33	<p>For a FET when will maximum current flows?</p> <ul style="list-style-type: none"> <li>• <math>V_{gs} = 0V</math></li> <li>• <math>V_{gs} = 0 V</math> and <math>V_{ds} \geq  V_p </math></li> <li>• <math>V_{ds} \geq  V_p </math></li> <li>• <math>V_{ds} = 0 V</math></li> </ul>	1	CO2
Q34	<p>FETs are ..... controlled device</p> <ul style="list-style-type: none"> <li>• Current</li> <li>• Voltage</li> <li>• both current and voltage</li> <li>• None of the above</li> </ul>	1	CO2
Q35	<p>The MOSFET stands for</p> <ul style="list-style-type: none"> <li>• Metal oxidized selenium FET</li> <li>• Metal oxide surface FET</li> <li>• Metal of surface FET</li> <li>• Metal oxide semiconductor FET</li> </ul>	1	CO2
Q36	<p>Choose the correct statement</p> <ul style="list-style-type: none"> <li>• "MOSFET is a unipolar, voltage controlled, two terminal device"</li> <li>• "MOSFET is a bipolar, current controlled, three terminal device"</li> <li>• "MOSFET is a unipolar, voltage controlled, three terminal device"</li> <li>• "MOSFET is a bipolar, current controlled, two terminal device"</li> </ul>	1	CO2
Q37	<p>Negative feedback.....</p> <ul style="list-style-type: none"> <li>• is same as the positive feedback</li> <li>• has no effect on gain of amplifier</li> </ul>	1	CO2

	<ul style="list-style-type: none"> <li>Increases the gain of amplifier</li> <li>Decreases the gain of amplifier</li> </ul>		
Q38	<p>The output of a particular op-amp increases 5V in 10 <math>\mu</math>s. The slew rate is .....</p> <ul style="list-style-type: none"> <li>5 v/<math>\mu</math>s</li> <li>0.5 V/<math>\mu</math>s</li> <li>5 V/ms</li> <li>0.5 V/ms</li> </ul>	1	CO3
Q39	<p>With 0 volts at both the input terminals of an op-amp. The output of op-amp should be:</p> <ul style="list-style-type: none"> <li>0 V</li> <li>equal to slew rate rating</li> <li>equal to CMRR rating</li> <li>equal to the voltage gain</li> </ul>	1	CO3
Q40	<p>A voltage follower amplifier configuration has a voltage gain of.....</p> <ul style="list-style-type: none"> <li>1</li> <li>infinity</li> <li>"2,00,000"</li> <li>-1</li> </ul>	1	CO3

SECTION B (60 marks)

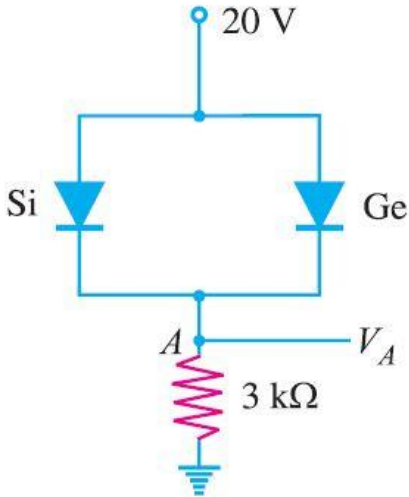Q1	<p>Calculate the current flowing through the silicon and germanium diodes if the circuit given below: Consider the forward voltage for Ge as 0.3 V and for Si as 0.7 V</p>  <p style="text-align: center;"> <ul style="list-style-type: none"> <li>Ge diode: 6.6 mA and Si diode: 0 mA</li> <li>Ge diode: 3.2 mA and Si diode: 3.2 mA</li> <li>Si diode: 6.4 mA and Ge diode: 0 mA</li> <li>Si diode: 3.3 mA and Ge diode: 3.3 mA</li> </ul> </p>	3	CO4
Q2	<p>An a.c. supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10:1. Find the</p>	3	CO4

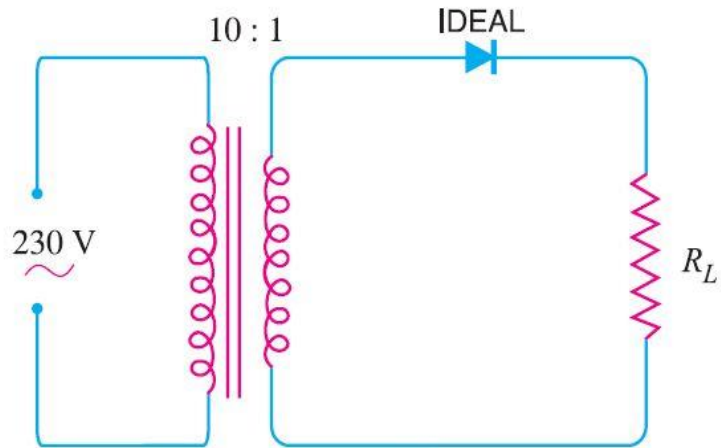
output d.c. voltage across Load resistance .



- 32.53 V
- 10.36 V
- 7.3 V
- 23 V

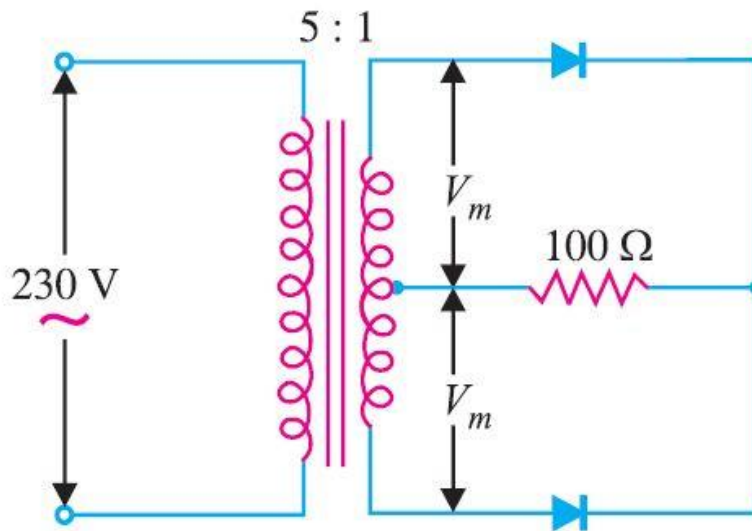Q3

For the rectifier circuit given below, calculate the d.c. output voltage:



- 46 V
- 20.7 V
- 29.27 V
- 65 V

3




CO4

Q4


For the zener diode configuration shown below:, calculate the voltage across 10KOhm resistor

3

C01

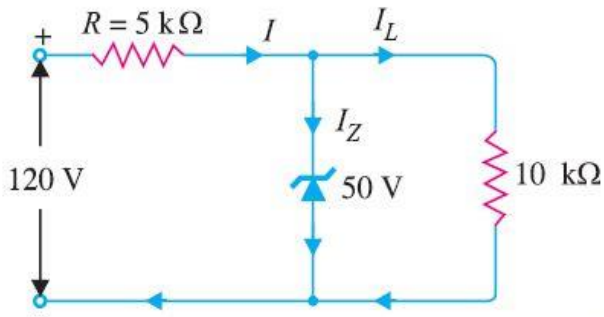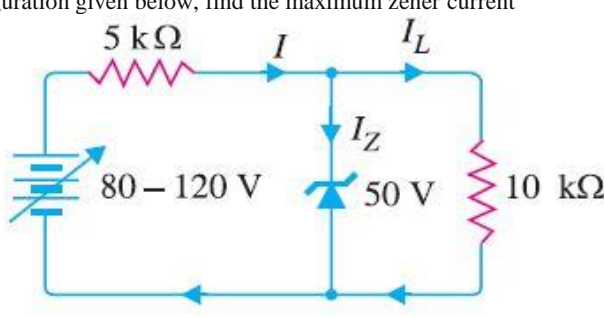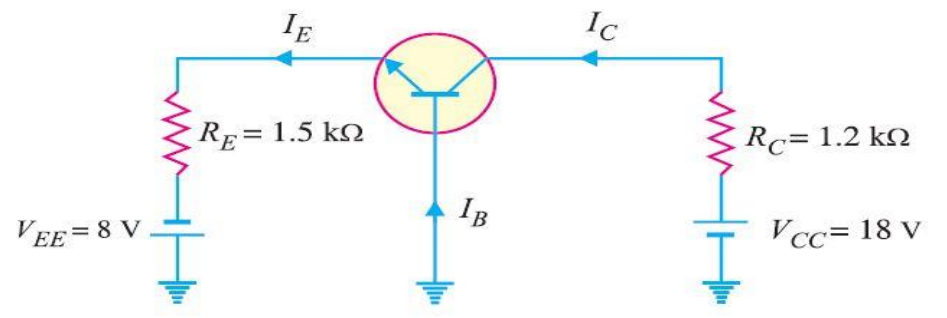
	 <ul style="list-style-type: none"> <li>• 50V</li> <li>• 70V</li> <li>• 80V</li> <li>• None of the above</li> </ul>		
Q5	<p>For the zener diode configuration given below, find the maximum zener current</p>  <ul style="list-style-type: none"> <li>• 1 mA</li> <li>• 5 mA</li> <li>• 9 mA</li> <li>• 14 mA</li> </ul>	3	CO4
Q6	<p>For the common base circuit shown below, determine the value of collector current.</p>  <ul style="list-style-type: none"> <li>• 4.87 mA</li> <li>• 5.3 mA</li> <li>• 6.08 mA</li> <li>• 6.7 mA</li> </ul>	3	CO4
Q7	Find the value of alpha for the transistor shown below:	3	CO4



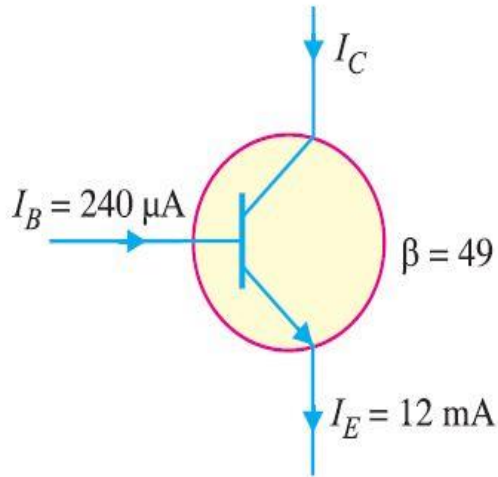


- 30.98
- 1
- 0.89
- 0.88

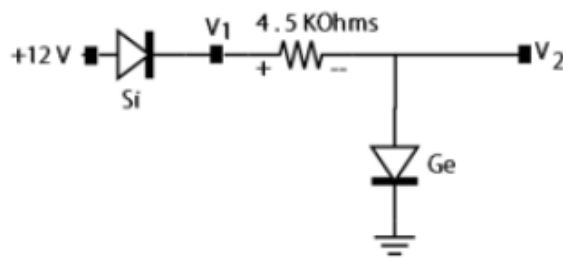Q8 For the circuit given in figure below, determine V1 and V2:



- V1 = 12 and V2 = 0.3
- V1 = 12 and V2 = 0
- V1 = 11.3 and V2 = 0.3
- None of the above

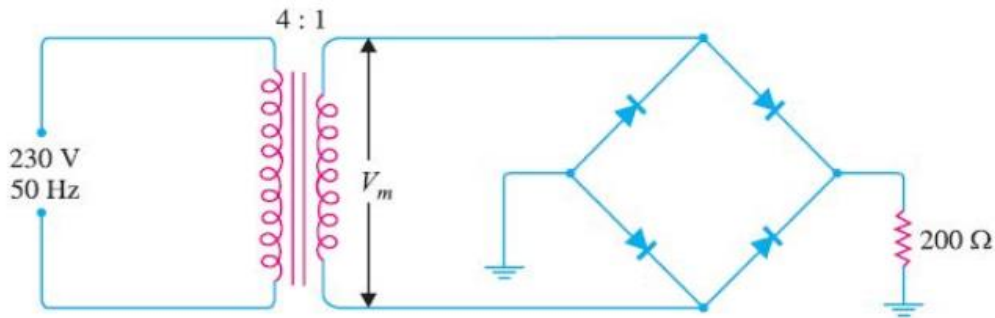Q9 in the bridge rectifier shown in the figure below, the diodes are assumed to be ideal. find the output DC voltage and frequency



- DC o/p voltage – 52 V and output frequency – 100 Hz
- DC o/p voltage – 52 V and output frequency - 50 Hz
- DC o/p voltage -57.5 V and output frequency 100Hz

3

CO4


3

CO4



- DC o/p voltage -57.5 V and output frequency - 50Hz

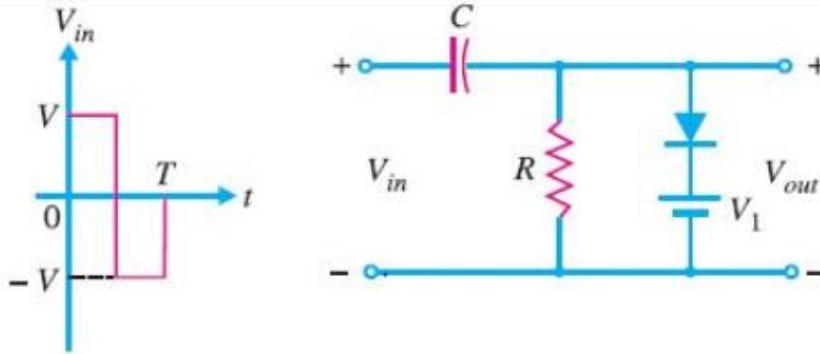Q10

Identify the output waveform for the following circuit with respect to given input waveform



Choices:

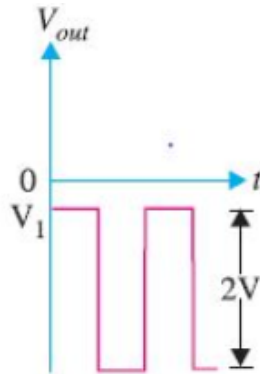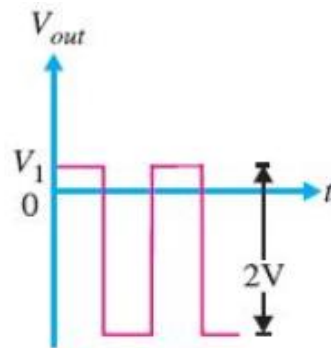

None of the above

Q11



For the following clipper circuit identify the output waveform with respect to the input waveform given below:

3


CO4

3




CO4

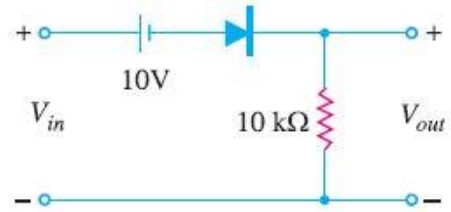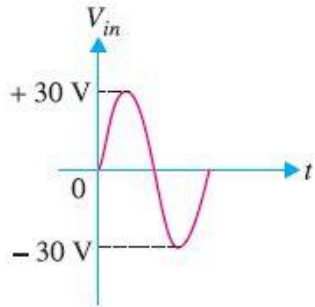

3 Choices:

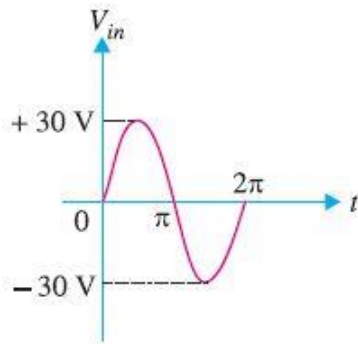

3

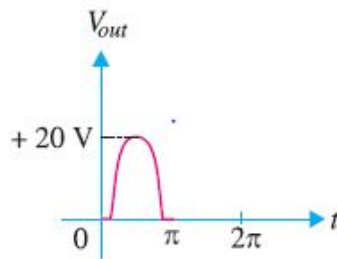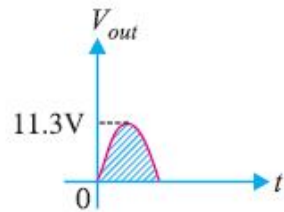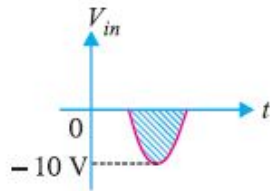


Q12

The transconductance curve for a JFET is given below, Determine the  $I_{DSS}$  from the

3

CO4

graph.

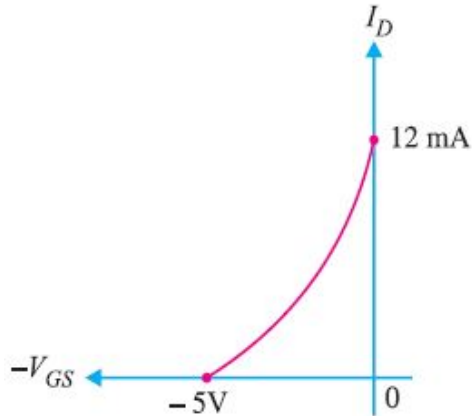

- -12 mA
- 0 mA
- -5 V
- 12 mA

Q13

A JFET has the following parameters:  $I_{DSS}=32\text{ mA}$ ,  $V_{GS(off)}=-8\text{ V}$ ,  $V_{GS}=-4.5\text{ V}$ . Calculate the value of drain current.


- 32 mA
- -6.12 mA
- -32 mA
- 6.12 mA

3

CO4

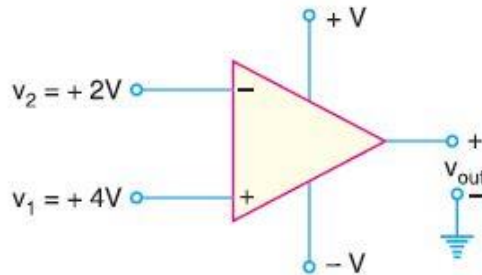Q14

For the op-amp configuration given below, calculate the output (assume gain=5 )



- 10 V
- -10 V
- 30 V
- -30 V

3


CO4

Q15

Calculate the output voltage for the following op-amp configuration. Assume the op-amp as 741C


3

CO4

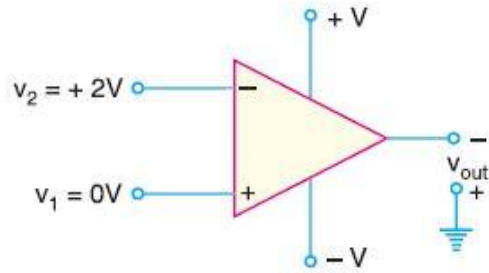


- 0.4 MV
- -0.4 MV
- $V_{sat}$
- $-V_{sat}$

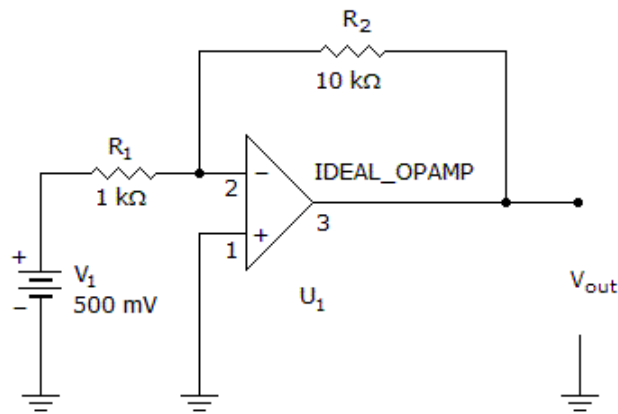Q16 What is the output Voltage for the given circuit?



- -5 V
- 5 V
- 10 V
- -10 V

Q17

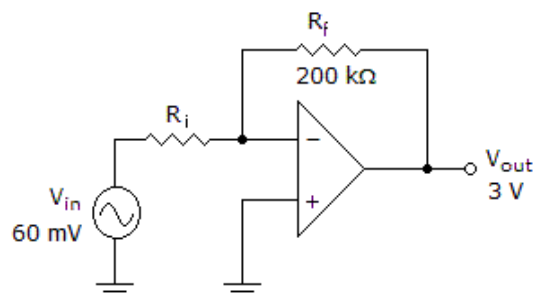



What value of input resistance is needed in the given circuit to produce the given output voltage?

- 50 Ohms
- 4 KOhms
- 40 KOhms
- 50 KOhms

Q18 For the circuit shown below, determine the magnitude of output voltage and identify the circuit

3


CO4

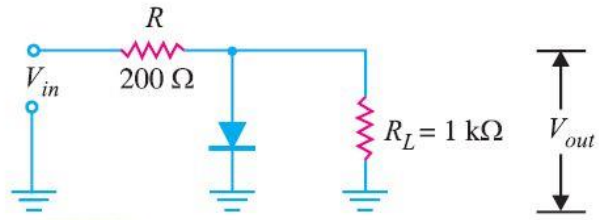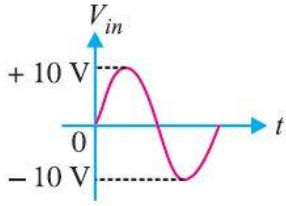

- negative shunt clipper  
For +ve half: 8.33 V  
For -ve half: 0.7 V
  
- positive shunt clipper  
For +ve half: 0.7 V  
For -ve half: 8.33 V
  
- negative shunt clipper  
For +ve half: 8.33 V  
For -ve half: 0.7 V
  
- positive shunt clipper  
For +ve half: 8.33 V  
For -ve half: 0.7 V

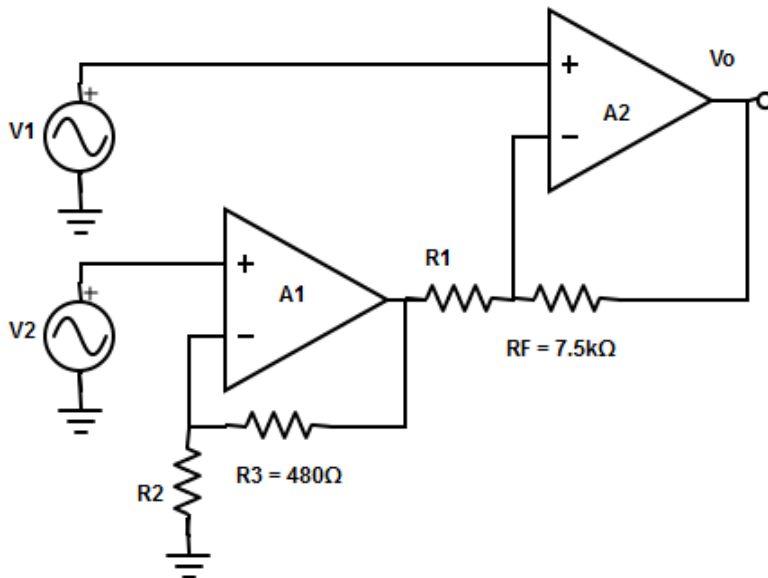Q19

Determine the output voltage from the diagram. Where  $V_1 = -4.3\text{Vpp}$  and  $V_2 = -5.1\text{Vpp}$  sinewave at 1KHz



- 12 Vpp sinewave at 1KHz
- 13.3 Vpp sinewave at 1KHz
- 14 Vpp sinewave at 1KHz


3

CO4

- 11 Vpp sinewave at 1KHz

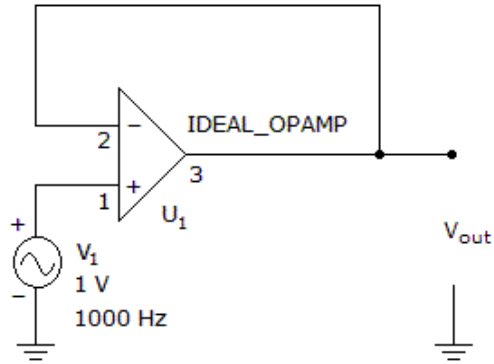Q20

What is the output waveform for the circuit given below?



- 1 V at 1 KHz
- 1 V at 1 KHz
- 10 V at 1 KHz
- 10 V at 1 KHz

3

CO4