

Name:	 <b>UPES</b> UNIVERSITY WITH A PURPOSE
Enrolment No:	

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**Online End Semester Examination, December 2020**

**Course: Digital systems and applications**  
**Program: BSc (H) Physics**  
**Course Code: PHYS 2003**

**Semester: III**  
**Time 03 hrs.**  
**Max. Marks: 100**

**SECTION A**

- 1. Each Question will carry 5 Marks**  
**2. Instruction: Complete the statements/Select the correct option/options.**

S. No.	Question	CO
Q1	Any three main advantages of an integrated circuit are _____, _____ and _____.	CO1
Q2	The decimal equivalence of binary number $(01011.1011)_2$ is _____	CO3
Q3	The various registers in 8085 are _____ a) Accumulator register and Temporary register b) Instruction register only c) Stack Pointer and Program Counter d) All of the above e) None of them	CO2
Q4	In any sequential logic circuit, output at any time depends only on input values of the _____ at that time. a) Past output values b) Intermediate value c) Both past output and present input d) Present input values e) None of the above	CO3
Q5	A bus is a group of conducting lines that carry _____, _____ and _____.	CO1
Q6	A full adder logic circuit normally will have _____ outputs and _____ inputs.	CO4

**SECTION B**

- 1. Each question will carry 10 marks**  
**2. Instruction: Write short/brief notes (maximum 200 Words).**

Q1	What is Race-around problem in JK Flip flop? How can you avoid it?	CO2
Q2	Write a short note on a multiplexer.	CO3

Q3	What are active and Passive Components? Explain the difference between them using suitable examples.	<b>CO1</b>
Q4	How do you construct a D-flip flop from SR flip-flop. Draw the circuit diagram of a D flip-flop using NAND configuration. Also make its truth Table.	<b>CO2</b>
Q5	What are counters? Differentiate between synchronous and asynchronous counters. Draw a circuit diagram of Ring counter using D-flip flop.  Or  Convert the $(154)_{10}$ to Binary system, Octal system and Hex system.	<b>CO3</b>
<b>SECTION-C</b>		
<b>1. Each Question carries 20 Marks.</b> <b>2. Instruction: Write long answer (maximum 500 Words).</b>		
Q1	What is a microprocessor? List any ten main features of 8085 IC.  Or  What are different types of memories? Classify memory devices and list their five main characteristics properties.	<b>CO2</b>