
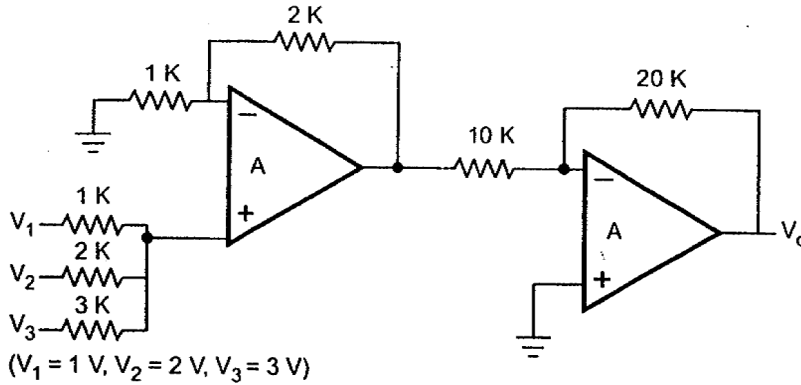


Name:			
Enrolment No:			
UNIVERSITY OF PETROLEUM AND ENERGY STUDIES End Semester Examination, December 2022			
Course: Analog System and Application Semester: III Program: B.Sc H (Physics) & Int. B.Sc. MSc. Physics Code: PHYS 2025			
		Time: 03 hrs. Max. Marks: 100	
Instructions: All questions are compulsory. Internal choices are given in Q6 and Q10			
SECTION A (5Qx4M=20Marks)			
S. No.		Marks	CO
Q 1	List the basic conditions to be satisfied for faithful amplification.	4	CO1
Q2	For an ideal Op-Amp, value of input impedance, bandwidth, offset voltage and open loop voltage gain are (a)....., (b)....., (c)....., and (d)..... respectively.	4	CO1
Q3	With the help of output characteristic curves of a common emitter amplifier, please define Active, Cutoff and Saturation regions.	4	CO1
Q4	State the law of mass-action and its significance.	4	CO1
Q5	Explain the principle and working of a solar cell in brief.	4	CO2
SECTION B (4Qx10M= 40 Marks)			
Q6	State the principle and working of a light-emitting diode (LED) with suitable diagrams. How are LEDs employed as power indicators and seven-segment displays? OR What is a ZENER diode and how is it used as a voltage regulator? (Use appropriate diagrams and expressions)	10	CO1
Q7	Draw the circuit diagram and explain the working of a RC coupled transistor amplifier. Also mention its advantages and disadvantages.	10	CO2
Q8	Explain the working of Hartley's oscillator with the help of a circuit diagram and also write the expressions for feedback and frequency fractions. What are the drawbacks of L-C based oscillators?	10	CO2
Q9	(a) A transistor uses voltage divider bias method, with $R_1 = 50 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$ and $R_E = 1 \text{ k}\Omega$, If $V_{CC} = 12 \text{ V}$ and $V_{BE} = 0.1 \text{ V}$, determine the value of I_c . (b) If negative voltage feedback fraction is 0.01 and gain after feedback is 50, the value of voltage gain without feedback will be.....	5 5	CO3

SECTION-C
(2Qx20M=40 Marks)

Q10

Calculate the output voltage in the following circuit:




20

CO3

OR

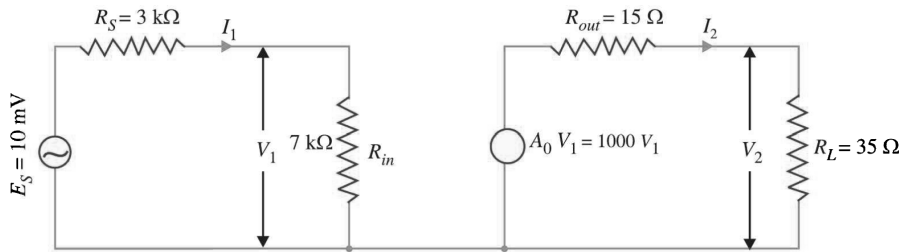An amplifier has an open circuit voltage gain of 1000, an output resistance of 15Ω and an input resistance of 7k Ω. It is supplied from a signal source of e.m.f. 10 mV and internal resistance 3k Ω. The amplifier feeds a load of 35Ω. Determine (i) the magnitude of output voltage, and (ii) power gain.



Q11

- (a) Analyse the circuit of a single stage common-emitter amplifier as a two port network using h-parameter model.
- (b) Design an operational amplifier circuit to be used as (a) a differentiator, and (b) an integrator.

10

5+5

CO4