
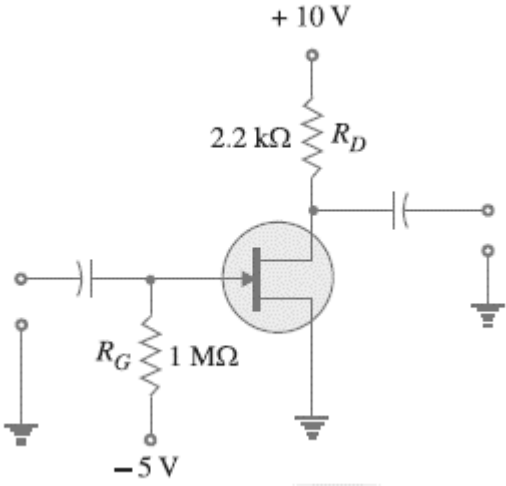
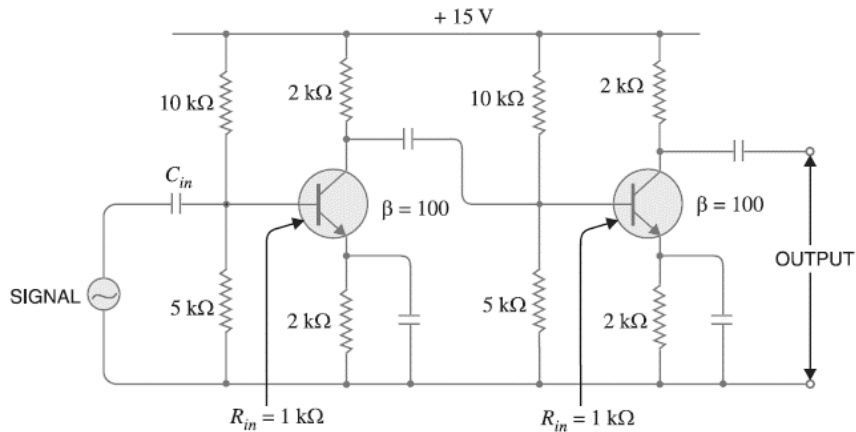


Name:			
Enrolment No:			
UNIVERSITY OF PETROLEUM AND ENERGY STUDIES End Semester Examination, December 2022			
Course: Analog Electronics		Semester: III	
Program: B.Tech Electrical Engg		Time : 03 hrs.	
Course Code: ECEEG 2027		Max. Marks: 100	
Instructions:			
SECTION A (5Qx4M=20Marks)			
S. No.		Marks	CO
Q1.	Define the amplification factor of a common base configuration if $I_C = 0.88 \text{ mA}$ and $I_B = 0.02 \text{ mA}$. Find the value of α	4	CO1
Q2.	Define base width modulation with help of a neat sketch.	4	CO2
Q3.	Write the Millers theorem and its characteristics with help of a circuit	4	CO2
Q4.	A JFET has the following parameters $I_{DSS} = 30 \text{ mA}$; $V_P(\text{off}) = -8 \text{ V}$; $V_{GS} = -4 \text{ V}$. Find the value of drain current	4	CO3
Q5.	Write about multistage amplifiers classification and frequency response of an amplifier.	4	CO4
SECTION B (4Qx10M= 40 Marks)			
Q6.	(a) Draw the Eber's Moll Model for Common Emitter Configuration and current equations in normal mode of operation. (b) In a common base connection, current amplification factor is 0.8. If the emitter current is 1mA, determine the value of base current.	10	CO2
Q7.	Derive the small signal model of JFET common source amplifier circuit.	10	CO3
Q8.	A JFET in Fig. has values of $V_P = V_{GS(\text{off})} = -8 \text{ V}$ and $I_{DSS} = 16 \text{ mA}$. Determine the values of V_{GS} , I_D and V_{DS} for the circuit. and the operating point	10	CO3

			
<p>Q9.</p>	<p>(a) A three-stage amplifier has a first stage voltage gain of 100, second stage voltage gain of 200 and third stage voltage gain of 400. Find the total voltage gain in dB</p> <p>(b) Discuss the purpose of biasing and operating point in transistor or JFET.</p> <p style="text-align: center;">(or)</p> <p>(c) Explain the working of Cascode amplifier and its applications.</p> <p>(d) Write about Darlington Pair and its applications.</p>	<p>5+5</p>	<p>CO4</p>
<p>SECTION-C (2Qx20M=40 Marks)</p>			
<p>Q10</p>	<p>(a) Derive the mathematical equation for reverse leakage current and show all the current components in common collector configuration. Explain the input output characteristics for the same.</p> <p>(b) Determine the values of Current gain A_I, R_i, Voltage gain A_v and Y_o for a Common base configuration circuit, if the h-parameters are $h_{fb} = -0.98$; $h_{ob} = 0.49 \mu A/V$; $h_{ib} = 21.6 \Omega$; $h_{rb} = 2.9 \times 10^{-6}$; $R_i = R_s = 1 K\Omega$; $R_L = 10 K\Omega$.</p> <p>Note: Draw the CB circuit with transistor and its h-parameter equivalent.</p>	<p>8+12</p>	<p>CO3</p>
<p>Q11</p>	<p>(a) Derive an expression for Step response applicable to any Amplifier.</p> <p>(b) Figure below shows two-stage RC coupled amplifier. If the input resistance R_{in} of each stage is $1 k\Omega$, Find (i) voltage gain of first stage (ii) voltage gain of second stage (iii) total voltage gain.</p>	<p>8+12</p>	<p>CO4</p>



(or)

(c) Derive an expression for lower and higher cutoff frequencies in a gain plot of an Amplifier.

(d) In an n-channel JFET biased by potential divider method, it is desired to set the operating point at $I_D = 2.5 \text{ mA}$ and $V_{DS} = 8 \text{ V}$. If $V_{DD} = 30 \text{ V}$, $R_1 = 1 \text{ M}\Omega$ and $R_2 = 500 \text{ k}\Omega$, find the value of R_S . The parameters of JFET are $I_{DSS} = 10 \text{ mA}$ and $V_{P} = V_{GS}(\text{off}) = -5 \text{ V}$.

