


Name: Enrolment No:	
--------------------------------------	--

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2022


Course: Electrical Power System-I
Program: B.Tech (RSEE)
Course Code: EPEG2018

Semester: III
Time: 03 hrs.
Max. Marks: 100


Instructions: Read the instructions provided for every question properly before attempting the answer. Use of calculator is permitted.

SECTION A
(5Qx4M=20Marks)

S. No.	Question	Marks	CO
Q 1	Briefly describe the major components of the power system.	4	CO1
Q 2	Determine the critical disruptive voltage and corona loss for a 3-phase line operating at 110 kV which has conductor of 1.25 cm dia arranged in a 3.05 metre delta. Assume air density factor of 1.07 and the dielectric strength of air to be 21 kV/cm.	4	CO2
Q 3	What is corona loss in transmission system?	4	CO4
Q 4	Explain with a suitable graph the behavior of cost versus transmission distance for both ac and dc type system.	4	CO1
Q 5	A conductor consists of seven identical strands each having a radius of r. Determine the factor by which r should be multiplied to find the self GMD of the conductor.	4	CO5

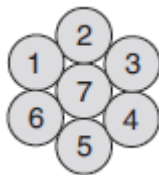

SECTION B
(4Qx10M= 40 Marks)

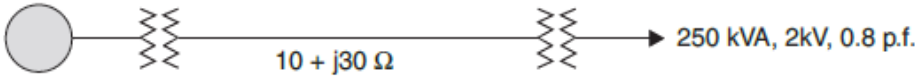Q 6	Determine the voltage at the generating station and the efficiency of transmission for the following 1-phase system:  Transformer ratio 2 kV/11 kV. The resistance on l.v. side = 0.04 ohm and h.v. side 1.3 ohm. Reactance on l.v. and h.v. side is 0.125 ohm and 4.5 ohm.	10	CO5
-----	---	----	-----

Q 7	A 400 V, 3-phase 4-wire service mains supplies a star connected load. The resistance of each line is 0.1 ohm and that of neutral 0.2 ohm. The load impedances are $Z_R = (6 + j9)$, $Z_Y = 8$ ohms and $Z_B = (6 - j8)$. Calculate the voltage across each load impedance and current in the neutral. Phase sequence RYB.	10	CO3
Q 8	Define Ferranti effect. Describe in detail the explanation of Ferranti-effect by considering lumped impedance and net reactive power flow on the line.	10	CO1
Q 9	Prove that the relation between the parameters of a two-terminal pair network is $AD-BC = 1$. OR Derive the expression of total flux linkage due to current flowing in a 1-phase two-wire transmission line.	10	CO2
SECTION-C (2Qx20M=40 Marks)			
Q 10	(a) The line-to-ground voltages on the high voltage side of a step-up transformer are 100 kV, 33 kV and 38 kV on phases a, b and c respectively. The voltage of phase a leads that of phase b by 100° and lags that of phase c by 176.5° . Determine analytically the symmetrical components of voltage. (b) The line currents in amperes in phases a, b and c respectively are $500 + j150$, $100 - j600$ and $-300 + j600$ referred to the same reference vector. Find the symmetrical component of currents.	10+10	CO4
Q 11	Determine the efficiency and regulation of a 3-phase, 100 km, 50 Hz transmission line delivering 20 MW at a p.f. of 0.8 lagging and 66 kV to a balanced load. The conductors are of copper, each having resistance 0.1 ohm per km, 1.5 cm outside dia, spaced equilaterally 2 metres between centres. Neglect leakance and use (i) nominal-T, and (ii) nominal- π method. OR Derive the expression of % regulation and efficiency for a medium transmission line for both nominal-T and nominal- π configurations.	20	CO3