

Name:	 <b>UPES</b> <small>UNIVERSITY WITH A PURPOSE</small>
Enrolment No:	

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, May 2023**

**Course: Digital Logic and Computer Organization**  
**Program: B.Tech CSE (All Batches)**  
**Course Code: CSEG 1015**

**Semester: II**  
**Time: 03 hrs.**  
**Max. Marks: 100**

**Instructions: There are three sections. Attempt all questions.**

**SECTION A**

**1. Each Question will carry 4 Marks**

S. No.	Question	Marks	CO
Q1	What are ripple counters? Why are they called so?	<b>3+1</b>	CO4
Q2	Convert the following numbers to their decimal equivalents: a) $F1792_{16}$ b) $56671_8$	<b>2x2</b>	CO1
Q3	Realise AND and OR operations through NAND and NOR gates.	<b>4</b>	CO2
Q4	Write a short note on TTL.	<b>4</b>	CO5
Q5	What are the different operations possible with JK Flip Flop? Support your answer with relevant state table.	<b>4</b>	CO4

**SECTION B**

**1. Each question will carry 10 marks.**

Q6	Simplify the following Boolean functions with the help of K-Map: a) $F(A,B,C)=\pi(0,3,6,7)$ b) $F(A,B,C,D)=\pi(3,5,7,8,10,11,12,13)$	<b>4+6</b>	CO2
Q7	Simplify the following function using Quine Mc'Clusky method: $F(A,B,C,D) = \sum m(0,1,2,4,6,8,9,11,13,15)$ .	<b>10</b>	CO2
Q8	Design a 4 bit BCD adder and explain its working logic starting from truth table.	<b>10</b>	CO3
	<b>OR</b>	<b>OR</b>	
	(a) Design a Decimal to BCD encoder with truth table and final logic diagram. (b) Design a 4X1 multiplexer with truth table and logic diagram.	<b>5+5</b>	

Q9	Design a 4 bit odd counter with T flip flops and give the relevant timing diagram.	<b>10</b>	CO4
<b>Section C</b>			
<b>1. Each question will carry 20 marks</b>			
Q10	What are the four different types of shift registers? Give a very brief description of each with respective circuit diagrams.	<b>20</b>	CO4
Q11	<p>What is a 555 timer? Why is it called so?</p> <p>Give a detailed operational description of astable multivibrator using LM555 timer with necessary diagrams, waveforms and equations.</p> <p style="text-align: center;"><b>OR</b></p> <p>Write short notes on:</p> <p>RAMs, ROM, EPROM, and EEPROM</p>	<p><b>3+2+15</b></p> <p><b>OR</b></p> <p><b>(4x5)</b></p>	CO6