

Name:			
Enrolment No:			
UPES			
End Semester Examination, December, 2023			
Programme Name: B Tech –Electronics and Computer Engineering		Semester : III	
Course Name : Analog Electronics		Time : 3 hr	
Course Code : ECEG-2048		Max. Marks: 100	
Nos. of page(s) : 02			
Instructions: Attempt all the sections.			
SECTION A (5Qx4M=20Marks)			
S. No.	Attempt all the questions.	Marks	CO
Q 1	What are the hybrid-parameters (h-parameters)? Explain.	4	CO1
Q2	Draw and analyze the I-V characteristics of Junction field effect transistor (JFET). Why the channel of JFET is never completely closed at the drain end?	4	CO1
Q3	A certain Junction field effect transistor (JFET) has a g_m of 4 mS. With an external drain resistance of 1.5kohm. Determine the value of ideal voltage gain.	4	CO2
Q4	Differentiate between positive and negative feedback amplifiers and explain their importance in electronic circuits	4	CO3
Q5	Discuss the key features and applications of a 555 timer IC in electronic circuits. Provide examples of where they are commonly used.	4	CO4
SECTION-B (4Qx10M= 40 Marks)			
Q 6	A bipolar junction transistor had the following h-parameters: $h_{ie} = 2000\Omega$; $h_{re} = 1.6 \times 10^{-4}$; $h_{fe} = 49$; $h_{oe} = 50\mu A/V$ Determine the current gain, voltage gain, input resistance and output resistance of the CE amplifier if the load resistance is 30 k Ω and source resistance is 600 Ω .	10	CO1
Q7	The pinch-down voltage of a P-channel junction FET is $V_p = 5V$ and the drain-to-source saturation current $I_{DSS} = -40mA$. The value of drain source voltage V_{DS} is such that the transistor is operating in the saturated region. The drain current is given as $I_D = -15mA$. Determine the gate-source voltage V_{GS} .	10	CO2

Q8	<p>Attempt both the parts:</p> <p>(a) Tuned collector oscillator uses an L-C tuned circuit having $L=29.3\mu\text{H}$ and $C=450\text{pF}$. Obtain the frequency of oscillation.</p> <p>(b) Analyze the Colpitt's oscillator circuit with suitable applications.</p>	3+7	CO3
Q9	<p>Show the connection of three op-amp stages using an LM-348 IC to provide outputs that are 10, 20, and 50 times larger than the input and 180° out of phase with respect to input. Use a feedback resistor of $R_f = 500k\Omega$ in all stages.</p>	10	CO4
<p>SECTION-C (2Qx20M=40 Marks)</p>			
Q 10	<p><u>Attempt both the parts</u></p> <p>(a) A negative feedback of $\beta= 0.002$ is applied to an amplifier of gain 1000. Calculate the change in overall gain of the feedback amplifier if the internal amplifier is subjected to gain reduction of 15%.</p> <p>(b) Describe the ideal characteristics of an op-amp and compare with the practical op-amp.</p>	10+10	CO3
Q11	<p><u>Attempt both the parts:</u></p> <p>(a) Describe the various operating modes of a 555 timer IC, including mono-stable, and bi-stable operation modes. Discuss the typical applications of a 555 timer IC in electronics and provide examples of projects where it can be used.</p> <p>(b) What is the purpose of an ADC in the context of electronics and signal processing? Design successive approximation ADC architectures, and provide examples of where each might be used.</p>	10+10	CO4