

Name:	
Enrolment No:	

UPES
End Semester Examination, December 2023


Program Name: Electronics & Communication Engineering/ Electronics & Computer Engineering Semester: III
Course Name: Digital System Design Time: 3 hrs
Course Code: ECEG-2037 Max. Marks: 100
Nos. of page(s): 2 Instructions: Assume any data in the design, if required.

SECTION-A (5Q x 4M = 20 Marks)

S. No.	Question	Marks	CO
Q.1	Explain the followings with example for digital logic families. (a) Fan-in (b) Fan-out (c) Propagation delay (d) Noise Margin (e) Power dissipation	5	CO4
Q.2	Discuss the functionality of JK flip-flop with truth table, characteristics table, equation and support design using NAND and NOR logic.	5	CO3
Q.3	Explain the functionality and logic diagram of the (3 x 8) decoder.	5	CO2
Q.4	Solve the following function minterms using 5-variable K-MAP directly or the Tabulation method. $f(A, B, C, D, E) = \sum (m_0, m_2, m_5, m_7, m_8, m_{10}, m_{16}, m_{21}, m_{23}, m_{24}, m_{27}, m_{31})$	5	CO1

SECTION B (4Q x 10M = 40 Marks)


Q.5	Design a code converter that accepts 4-bit gray code as inputs and provides 4-bit binary output.	10	CO2
Q.7	Detail the ECL logic family for non-saturated logic with complete description of the logic circuit and operation. How is it applicable for wired logic, AND, and OR operation? <p style="text-align: center;">OR</p> Design a 4-bit multiplier with complete description of functionality, truth table, and logic diagram that accepts two inputs. Input $A = A_3 A_2 A_1 A_0$ input $B = B_3 B_2 B_1 B_0$	10	CO4
Q.8	What is the difference between Mealy and Moore FSM? The state diagram of a Moore FSM is shown. Design the FSM using D/JK flip-flop.	10	CO3

 

Q.9

A sequential circuit is defined using the following logic diagram. Determine the following.

 - (a) State transition equations
- (b) State Table
- (c) State diagram



10

CO3

SECTION-C (2Q x 20M = 40 Marks)

Attempt any two of the following

Q.10

Convert/implement the following.

- (a) JK flip-flop to D Flip-Flop
- (b) D- Flip-Flop to T-flip-flop
- (c) Full adder using the decoder
- (d) Multiplexer (16x1) using (4x1) multiplexer

20

CO2

Q.11

(a) Compare the functionality of PAL, PLA, and PROM technology for PLDs. Implement the full subtractor function using PAL, PLA, and PROM.

(b) Design BCD Adder using 4-bit binary adder and detail the complete behavior with equation and truth table

10+10

CO1

Q.12

(a) Design a mod-12 synchronous counter using JK Flip-Flop.

(b) What are the different operations of the shift register? Detail the operation of the 4-bit shift register, logic diagram with timing diagram for any one operation.

15+5

CO3